

LECTURE NOTES
ON
NETWORK THEORY
3rd SEMESTER
JYOTI PRAKASH JENA
ASST. PROFESSOR
DEPARTMENT OF ELECTRICAL ENGINEERING



GANDHI INSTITUTE OF TECHNOLOGY AND MANAGEMENT(GITAM)

Affiliated to BPUT & SCTE&VT, Govt. of Odisha



Approved by AICTE, New Delhi



Superposition Theorem

In a linear bilateral network containing more than one source of energy the overall effect of all sources considered simultaneously is same as the algebraic sum of individual effect of each source considered one at a time and being independent of all other sources

Explanation

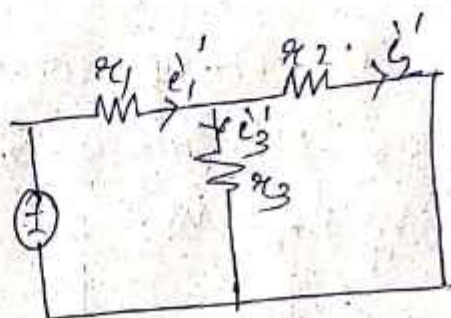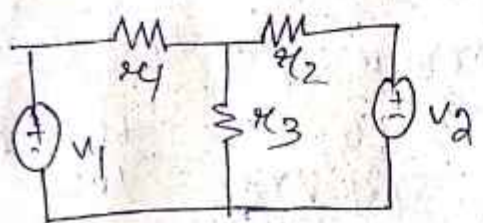


$$i_1' = \frac{V_1}{\frac{R_1 R_2 R_3}{R_2 + R_3} + R_1}$$

$$\text{Again } i_2' = i_1' \frac{R_2}{R_2 + R_3}$$

$$i_3' = \cancel{i_1'} - i_2'$$

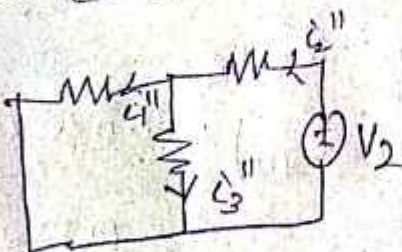Next by removing V_1 by short circuit, let the circuit be energized by V_2 only



$$i_2'' = \frac{V_2}{\frac{R_1 R_2 R_3}{R_1 + R_3} + R_2}$$

$$i_3'' = i_2'' \frac{R_3}{R_1 + R_3}$$


$$i_3'' = i_2'' - i_1''$$

As per superposition


$$i_3 = i_3' + i_3''$$

* Direction of current calculated of each source should be taken care of)

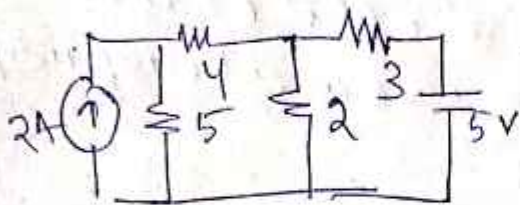Ex Find the current flowing in the 2Ω resistor of the circuit shown in fig by applying superposition theorem




Sol By using source conversion

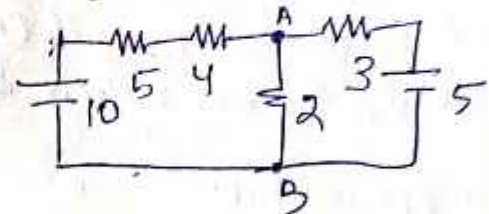

S-1 Consider voltage source 10V only

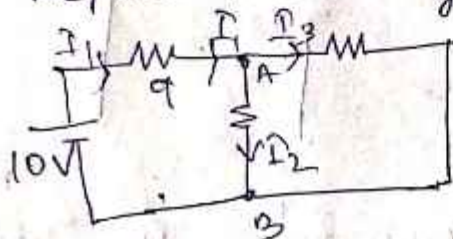Replace the voltage (5V) source by a short circuit




$$I_1 = \frac{10}{9 + \frac{2 \times 3}{2+3}} = \frac{10}{10.2} = 0.98 \text{ A}$$

By current division rule.

$$I_2 = I_1 \left(\frac{3}{3+2} \right) = 0.98 \times \frac{3}{5} = 0.58 \text{ A}$$

S-2 Consider voltage source 5V only

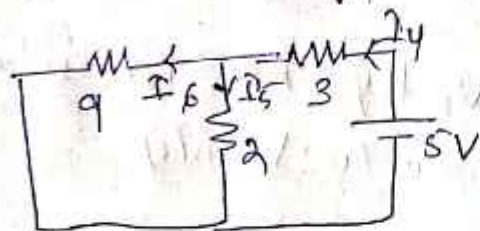

$$I_4 = \frac{5}{3 + \left(\frac{2 \times 9}{2+9} \right)} = \frac{5}{4.636} = 1.078 \text{ A}$$

By current division. Rule.



$$I_5 = I_4 \left(\frac{9}{2+9} \right) = 1.078 \times \frac{9}{11} = 0.882 \text{ A}$$

(From A to B)

S-3 According to superposition theorem

Total current in 2Ω resistor due to the presence of both source below $(I_2 + I_5) = 1.47 \text{ A}$
(From A to B)

Thevenin's Theorem

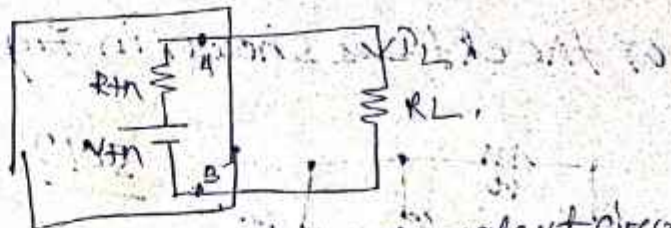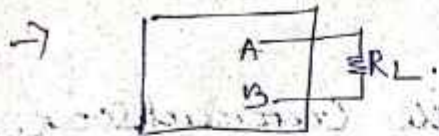

of general network (Thevenin equivalent circuit)

$$I_L = \frac{V_{th}}{R_{th} + R_L}, \quad V_{AB} = I_L R_L$$

Statement

In order to find the response through any particular element connected across a pair of terminal A & B of a linear active network the rest of the network may be replaced by a Thevenin voltage (V_{th}) & a series resistance called thevenin's resistance (R_{th}).

Procedure

S-1 Replace current source if any with equivalent voltage source.

S-2 Identify a pair of terminal A & B across the desired element and mark it as R_L .

S-3 Find voltage across A & B in absence of R_L and mark as V_{th} .


S-4 Replace all the voltage source with short circuit. Calculate the equivalent resistance by looking into the network from the open terminal A & B and mark this as R_{th} .

S-5 Draw Thevenin equivalent circuit.


S-6 Solve for current and voltage as per equation

$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad V_{AB} = I_L R_L$$

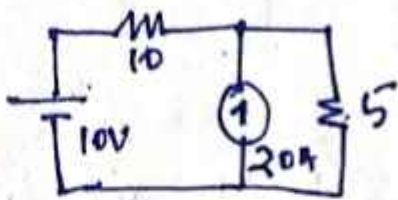
Ex: Find the current flowing in the 10Ω resistor of the ckt as shown in fig.



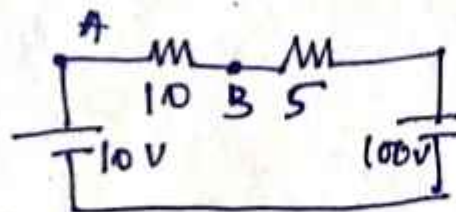Sol: Replace current source with equivalent voltage source.




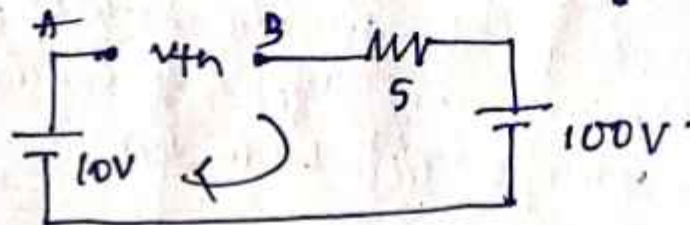Then 10Ω is removed from the circuit and its open terminals are marked as A & B.



Applying KVL $V_{th} = V_{AB} = -10 + 100 = 90V$

Calculation of R_{th}

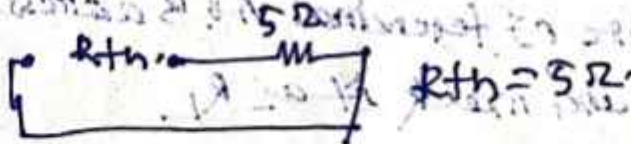


The th in equivalent ckt



$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{90}{10 + 5} = \frac{90}{15} = 6 \text{ Amp}$$

Norton's theorem

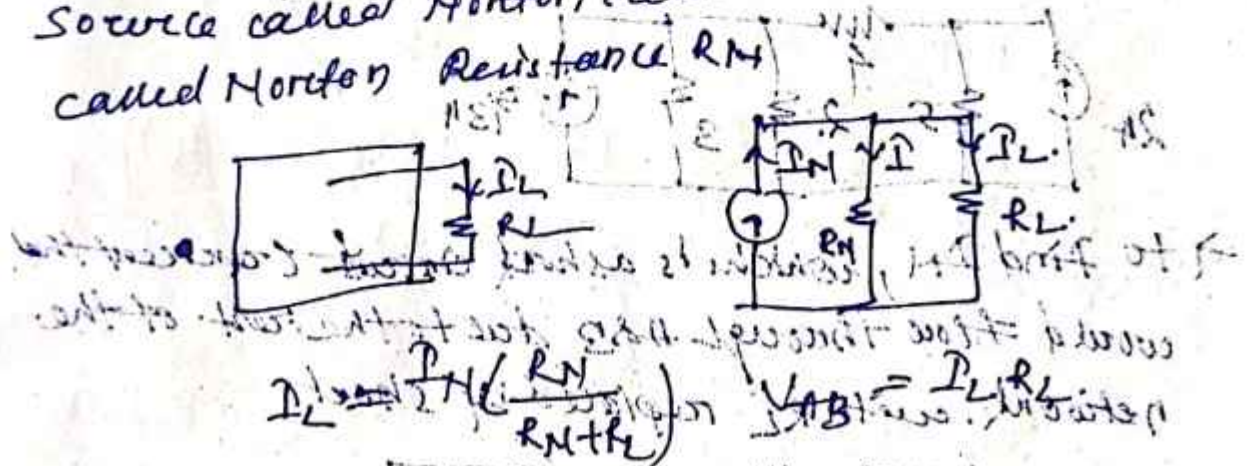statement → In order to find the response through any particular element connected across a pair of terminals A & B of a linear active D.C. Network the rest of the network may be replaced by a Norton equivalent circuit containing a current source called Norton current I_N & a resistor called Norton Resistance R_N .




Procedure

- Replace voltage source with only equivalent current source.
- Identify a pair of terminal A & B across the desired element and mark it as R_{AB} .
- Find the current that would flow through a shorted link replacing R_{AB} and mark it as I_N .
- Replace all current source with open circuit & calculate the equivalent resistance by looking into the network from the open terminal A & B and mark the R_N .
- Draw equivalent resistance.
- Solve the circuit and voltage as per eq 2

$$I_L = I_N \left(\frac{R_N}{R_N + R_L} \right) \quad V_{AB} = I_L R_L$$

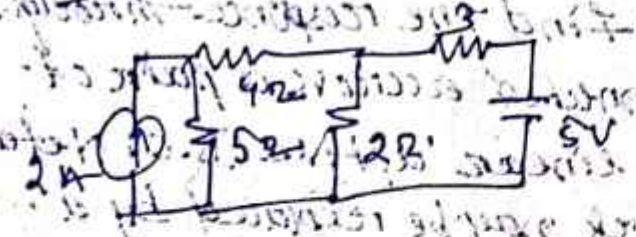
Qr Determine the current through a 2 resistor by applying thevenin theorem



Convert voltage source into current source.




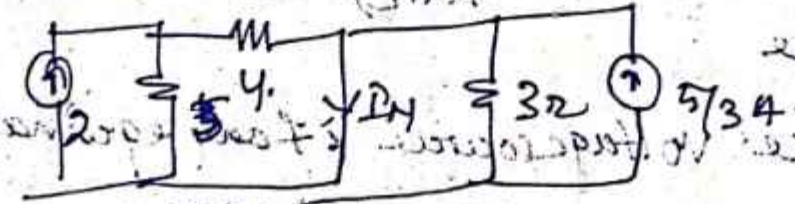→ to find I_L , which is a short circuit. Concept that would flow through R_{L} due to the rest of the network with R_L replaced by short.




$$I_{sc} = 2 \left(\frac{5}{5+1} \right) + \frac{5}{3} = 2.77 \text{ Amp}$$

Calculation of R_N

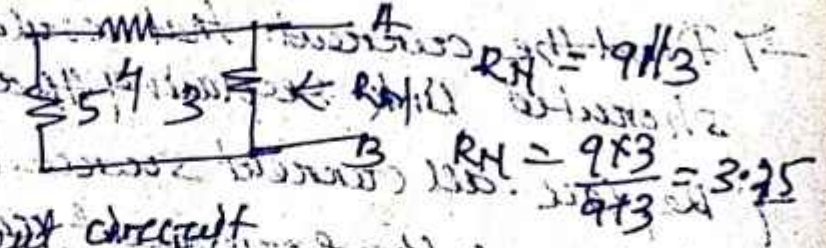

Norton equivalent circuit

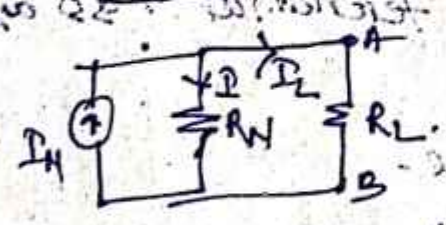


$$I_L = I_{sc} \left(\frac{R_N}{R_N + R_L} \right) = 2.77 \left(\frac{9/3}{9/3 + 2} \right) = 1.34 \text{ Amp}$$



∴ hence 1.34 Amp pass through R_L by Norton theorem

$$I_L = 1.34 \text{ Amp}$$

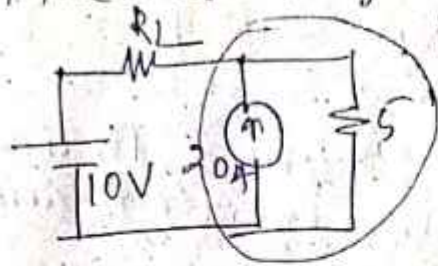Ex-2) Find the current flowing in the 10Ω resistor of the circuit by Norton's theorem.



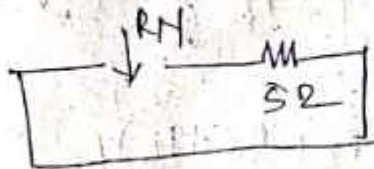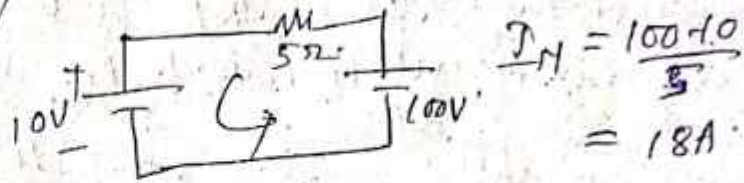→ $\frac{50V}{5\Omega}$ convert current source to voltage source



$$R_N = 5\Omega$$

Norton equivalent


$$I_L = I_N \left(\frac{R_N}{R_N + R_L} \right)$$

$$= 18 \left(\frac{5}{5 + 10} \right) = 6A$$



Maximum Power Transfer theorem

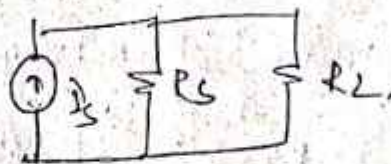→ In a linear bilateral network containing an independent voltage source in series with resistance (R_S) deliver max power to the load resistance (R_L) when R_L is equal to R_S . ($R_S = R_L$)



→ Similarly the independent current source parallel resistor source resistance R_S delivers max power to the load resistance $R_L = R_S$

→ Let's consider the above circuit

$$I = \frac{V_S}{R_S + R_L} \quad \text{--- (1)}$$

Power delivered to the $P_L = I^2 R_L$ — (2)

$$= \left(\frac{V_s}{R_s + R_L} \right)^2 R_L \quad \text{--- (3)}$$

to find the value of R_L for max^m power transfer differentiate P_L w.r.t R_L and equate to zero

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left\{ \left[\frac{V_s}{R_s + R_L} \right]^2 \cdot R_L \right\} \quad \text{--- (4)}$$

$$= V_s^2 \left[\frac{(R_s + R_L)^2 - 2R_L(R_s + R_L)}{(R_s + R_L)^4} \right] = 0 \quad \text{--- (5)}$$

$$\Rightarrow (R_s + R_L)^2 = 2R_L(R_s + R_L) \quad \text{--- (6)}$$

$$\Rightarrow R_s + R_L = 2R_L \quad \text{--- (7)}$$


$$\Rightarrow \boxed{R_s = R_L} \quad \text{--- 8}$$

We can find that max^m power

$$P_{max} = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_{th}$$

$$= \frac{V_{th}^2}{4R_{th}}$$

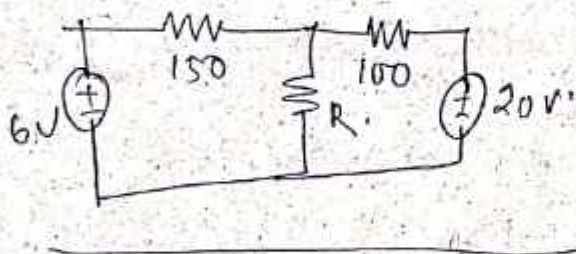
Q: Find the value of R for max^m power transfer



Solⁿ open circuit the resistance R and find V_{th} & R_{th} .

Apply KVL to the loop


$$6 - 150I - 100I - 20 = 0$$

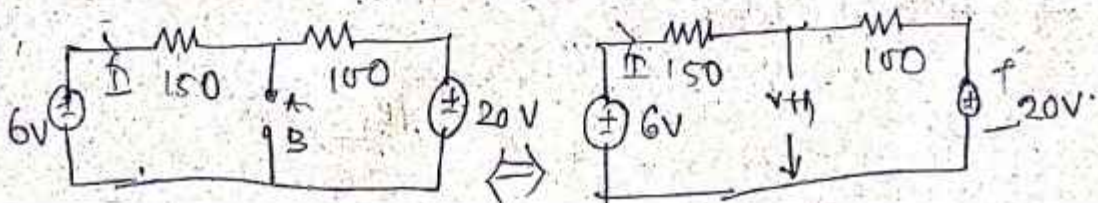

$$-250I = 14$$


$$I = \frac{-14}{250} = \frac{-7}{125} \text{ Amp}$$
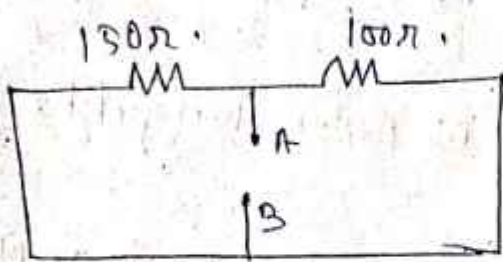
$$V_{th} = V_{AB} = 100I + 20 = 100 \left(\frac{-7}{125} \right) + 20 = 14.4 \text{ V}$$




To find R_{th} short circuit the voltage source and simplify to get

$$R_{th} = 60\Omega$$

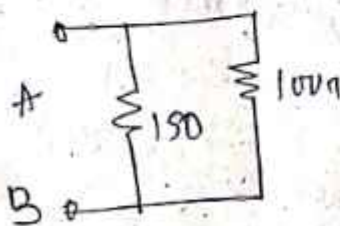


=

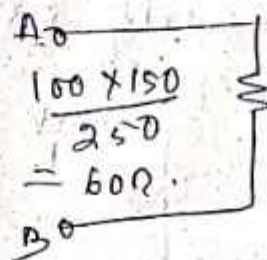

For Maximum power transfer

$$R = R_{th} = 60\Omega$$
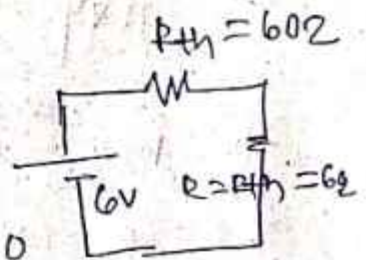
$$P_{max} = I^2 R = \left(\frac{14.4}{60+60} \right)^2 \times 60$$



* This theorem is not applicable if there are 2 or more source in a network in series or parallel.

Reciprocity theorem

statement \rightarrow If a source of emf located at one point in a network composed of linear ^{bilateral} network circuit elements produced a current I at a selected point in the network. The same source of emf acting at the 2nd point will produce the same current at the first point.

Procedure.

S-1 - The branch between which reciprocity theory is to be applied is selected first.

S-2. → The current in the branch is obtained using ^{conventional} network analysis ~~reciprocity theory~~ ~~is to be applicable~~.

S-3. - The voltage source is interchanged between the branch concerned.

S-4. The current in the branch where voltage source existing earlier is calculated.

Prob.




Ans $R_{eq} = \{ (2+1) \parallel 3 \} + 2 = \frac{9}{6} + 2 = \frac{21}{6} = 3.5$

$$I = \frac{V}{R_{eq}} = \frac{10}{3.5} = \frac{20}{7} \text{ Amp}$$

$$I_2 = I \times \frac{3}{3+1+2} = \frac{20}{7} \times \frac{3}{6} = \frac{10}{7} \text{ Amp}$$

Fig. 2.

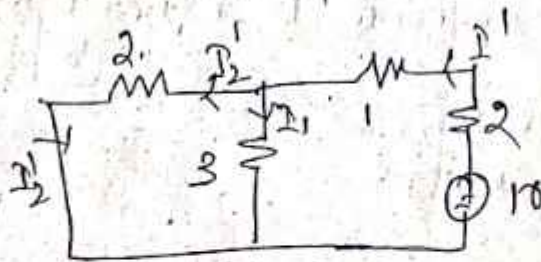

$$R_{eq} = (2 \parallel 3) + 1 + 2 = 6/5 + 3 = 21/5$$

$$I_1 = \frac{V}{R_{eq}} = \frac{10}{21/5} = \frac{50}{21}$$


$$I_2'' = \frac{50}{21} \times \frac{3}{3+2} = \frac{10}{7} \text{ Amp}$$

Application of Reciprocity Theorem

- This theorem is applicable to linear, time invariant n/w consisting of passive n/w elements
- This theorem is applicable in dc as well as ac circuit.
- This theorem allows interchange the position of excitation and response.
- It provide bilateral property of the network
- It provide great convenience in design and measurement.


Compensation Theorem

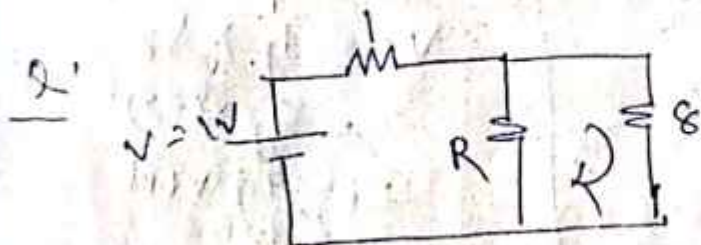In any linear bilateral active network, if any branch carrying a current I has its impedance Z changed by an amount δZ the resulting changes that occurs in the other branches are the same as those which would have been caused by the injection of a voltage source of $(-I \delta Z)$ in the modified branch.



$$4 - 2 = 2$$

(0.1) step

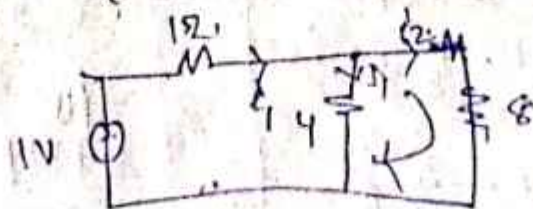

$$I = I_1 - I_2$$

Apply KVL in Loop-1

$$\begin{aligned}
 -e_1 - 4(e_1 - e_2) + 1 &= 0 \\
 \Rightarrow -e_1 - 4e_1 + 4e_2 &= -1 \\
 \Rightarrow -5e_1 + 4e_2 &= -1 \\
 \Rightarrow 5e_1 - 4e_2 &= 1 \quad \text{--- (1)}
 \end{aligned}$$

Apply KVL in Loop-2


$$\begin{aligned}
 -8e_2 + 4(e_1 - e_2) &= 0 \\
 \Rightarrow -8e_2 + 4e_1 - 4e_2 &= 0 \\
 \Rightarrow 4e_1 - 12e_2 &= 0 \\
 \Rightarrow -4e_1 + 12e_2 &= 0 \quad \text{--- (2)}
 \end{aligned}$$

Solving eqⁿ (1) & (2)

$$\begin{aligned}
 5e_1 - 4e_2 &= 1 \quad \text{--- (1)} \\
 -4e_1 + 12e_2 &= 0 \quad \text{--- (2)} \\
 e_1 &= \frac{3}{11} A \quad e_2 = \frac{1}{11} A
 \end{aligned}$$

$$I_1 = e_1 - e_2 = \frac{3}{11} - \frac{1}{11} = \frac{2}{11} \text{ Amp}$$

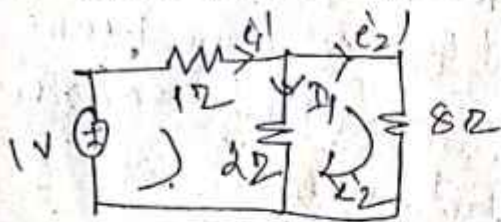Step-2, After changing the value of the resistance from 4Ω to 2Ω



$$\begin{aligned}
 I_1' &= e_1' - e_2' \\
 3e_1' - 2e_2' &= 1 \quad \text{--- (3)} \\
 -2e_1' + 10e_2' &= 0 \quad \text{--- (4)}
 \end{aligned}$$

By solving eqⁿ (3) & (4)

$$\begin{aligned}
 e_1' &= \frac{5}{13} A \quad e_2' = \frac{1}{13} A \\
 I_1' &= e_1' - e_2' = \frac{4}{13} A
 \end{aligned}$$

Change in current

$$\begin{aligned}
 \Delta I &= I_1' - I_1 \\
 &= \frac{4}{13} - \frac{2}{11} = \frac{18}{143} \text{ Amp}
 \end{aligned}$$

Using compensation theorem

$$\begin{aligned}
 V_C &= I_1 \times \Delta R \\
 &= \frac{2}{11} \times (-2) \\
 &= \left(-\frac{4}{11}\right) \text{ Volt}
 \end{aligned}$$

$$\begin{aligned}
 \Delta I &= \frac{-V_C}{2 + \frac{8}{9}} \quad \text{Equivalent Resistor} \\
 &= \frac{4/11}{2 + 8/9} = \frac{18}{143} \text{ Amp}
 \end{aligned}$$

Hence proved.

Table of dual element

Electrical Resistance \rightarrow Conductance.

Inductance \rightarrow Capacitance.

Capacitance \rightarrow Inductance.

Series Branch \leftrightarrow Parallel Branch.

Switch closed \rightarrow Switch open.


Charge \rightarrow Flux linkage.

Mesh \rightarrow Node.

Module-2

1st order circuit \rightarrow It contains resistance and one energy storing element i.e. one inductor or capacitor. This 1st order circuit, during its transient state of operation is governed by 1st order linear differential eqn.

R-L circuit

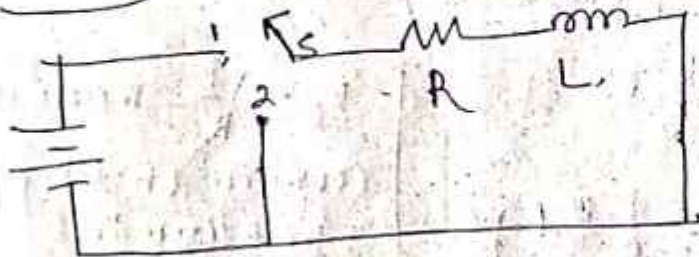

Consider some instant t seconds after the voltage is applied.
 $i =$ Current flowing through the circuit at instant t second

$\frac{di}{dt}$ = rate of growth of (current) at that instant

$$V_R = iR = \text{voltage across } R$$

$$V_L = L \frac{di}{dt} = \text{voltage across } L$$

Applying KVL $V = Ri + L \frac{di}{dt}$

$$\Rightarrow \frac{di}{dt} + \frac{R}{L}i = \frac{V}{L} \quad (1)$$

\Rightarrow eqn (1) is a non homogeneous eqn

So $i = e^{-\frac{R}{L}t} \int e^{\frac{R}{L}t} \cdot \frac{V}{L} dt + k e^{-\frac{R}{L}t}$ (2)

$$\Rightarrow i = i_p + i_c$$

Sol of eqn (2) is $i = \frac{V}{R} + k e^{-\frac{R}{L}t}$

At $t=0$ (just after switching) eqn (3) becomes

$$0 = \frac{V}{R} + k e^{-\frac{R}{L} \times 0} = \frac{V}{R} + k$$

$$k = -\frac{V}{R}$$

Putting in eqn (3) we get

$$i = \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$

$$\Rightarrow i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$i = I_0 (1 - e^{-t/\tau})$$

$$I_0 = \frac{V}{R} = \text{maximum}$$

current or steady
state current

$$\tau = \frac{L}{R} = \text{time constant}$$

we put $t = \tau = \frac{L}{R}$ in eqn (4) we get

$$i = I_0 (1 - e^{-1}) = 0.632 I_0 = 63.2\% \text{ of } I_0$$

we put $t = \infty$ in eqn (4) we get

$$i = I_0 (1 - e^{-\infty/\tau}) = I_0$$

Thus current in R-L circuit would attain max value (I_0) only after infinite time.

voltage drop across inductor $V_L = L \frac{di}{dt}$

$$\Rightarrow V_L = L \frac{d}{dt} [I_0 (1 - e^{-t/\tau})] = L \frac{d}{dt} [I_0 - I_0 e^{-t/\tau}]$$

$$\Rightarrow V_L = L \left[\frac{d}{dt} I_0 - \frac{d}{dt} I_0 e^{-t/\tau} \right] = L \left[0 + \frac{1}{\tau} I_0 e^{-t/\tau} \right]$$

$$\Rightarrow V_L = L \left[\frac{1}{\tau} I_0 e^{-t/\tau} \right] = I_0 R e^{-t/\tau}$$

$$\boxed{V_L = V e^{-t/\tau}} \quad \boxed{\text{where } V = I_0 R}$$

voltage drop across resistor is

$$V_R = iR = I_0 (1 - e^{-t/\tau}) R = V (1 - e^{-t/\tau})$$

→ In transient period voltage across resistor exponent rising and voltage across inductor exponentially decays. Once the transient dies out within a short time the steady current ($I_0 = V/R$) remains in the circuit.

R.C

Case-1 (charging of R.C circuit)



Consider a R-C circuit connected in series with a battery of voltage V and a switch 'S'.

→ Initially capacitor is uncharged and voltage across it is zero ($V_C = 0$)

⇒ $V_R = V$ → whole supply voltage.

Initial current in the circuit $I_0 = \frac{V}{R}$

→ As current flows in the capacitor starts charging and capacitor voltage V_C increases.

→ Consider some instant t second after the voltage is applied

i → current flowing through the circuit at instant t second.

$$V_R = Ri = \text{voltage drop across } R$$

$$V_C = \frac{1}{C} \int I \cdot dt = \text{voltage across } C$$

$$\text{Applying KVL } \boxed{Ri + \frac{1}{C} \int i \cdot dt = V}$$

Differentiating both sides w.r.t time t we get

$$R \cdot \frac{di}{dt} + \frac{i}{C} = 0 \Rightarrow \boxed{\frac{di}{dt} + \frac{1}{RC} i = 0} \quad \text{--- (1)}$$

Eqn) is a homogeneous eqⁿ solⁿ of the eqⁿ (1)

$$i = k e^{-t/RC} \quad \text{--- (2)}$$

where k is a constant, whose value can be calculated from the initial condition.

$$t = 0^+$$

$$\text{current } i(0^+) = \frac{V}{R}$$

$$\text{eqⁿ (2) becomes } \boxed{\frac{V}{R} = k e^{-t/RC}}$$

$$\Rightarrow \boxed{k = \frac{V}{R}}$$

Putting this value of ' k ' in eqⁿ (2)

$$i = \frac{V}{R} e^{-t/RC}$$

$$\Rightarrow \boxed{i = I_0 e^{-t/\tau}} \quad \text{--- (3)}$$

$$I_0 = \frac{V}{R} \text{ (max^m current in the circuit)}$$

$$\tau = RC \text{ (time const. or capacitive time constant)}$$

voltage across the resistor

$$V_R = iR = I_0 R e^{-t/\tau} = V e^{-t/\tau} \quad \text{--- (4)}$$

voltage across the capacitor

$$V_C = \frac{1}{C} \int i dt = \frac{1}{C} \int_0^t I_0 e^{-t/\tau} dt$$

$$\Rightarrow \boxed{V_C = V (1 - e^{-t/\tau})} \quad \text{--- (5)}$$


→ The charge stored in capacitor decreasing, charging

$$q = CV_c = CV(1 - e^{-t/\tau})$$


$$= Q(1 - e^{-t/\tau})$$

If we put $t = \tau = RC$, we get
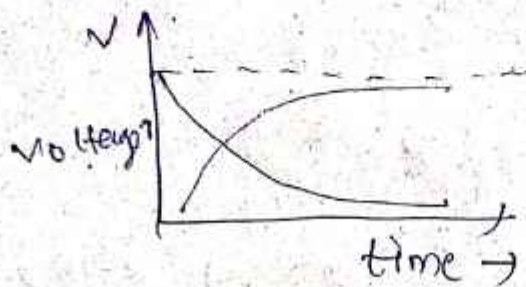
$$V_c = V(1 - e^{-1}) = 0.632V = 63.2\% \text{ of } V$$



Discharging of R.C circuit

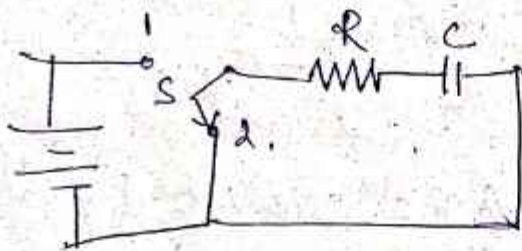

$i =$ discharging current at any instant

Applying KVL

$$Ri + \frac{1}{C} \int i \cdot dt = 0$$

Differentiating both sides w.r.t we

$$R \frac{di}{dt} + \frac{i}{C} = 0 \quad \text{--- (6)}$$

Eqn (6) is a homogenous differential eqn

$$i = K e^{-t/RC} \quad \text{--- (7)}$$

where K is a const., whose value can be calculated from initial condition


$$t = 0 \quad i = -V/R \quad \text{eqn (7) becomes}$$

$$-\frac{V}{R} = ke^{\frac{t}{RC}}$$

$$\Rightarrow \boxed{K = -\frac{V}{R}} \quad \text{Putting this value in eqn (1)}$$

$$i = -\frac{V}{R} e^{-t/RC} = -I_0 e^{-t/\tau}$$
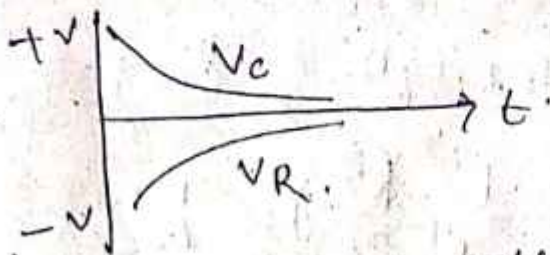
$$\boxed{i = I_0 e^{-t/\tau}} \quad \text{--- (8)}$$



$$V_R = Ri = -I_0 R e^{-t/RC} = -V_0 e^{-t/\tau}$$

$$V_C = \frac{1}{C} \int i dt = \frac{1}{C} \int -I_0 e^{-t/\tau}$$


$$\boxed{V_C = I_0 R e^{-t/\tau} = V_0 e^{-t/\tau}}$$

The charge on capacitor during discharging is

$$q = CV_C = C V_0 e^{-t/\tau} = Q_0 e^{-t/\tau}$$

$Q_0 = CV = \text{max}^m \text{ charge in capacitor.}$

R-L-C

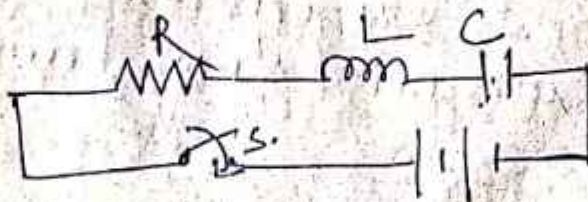

Applying KVL

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$\Rightarrow R \cdot \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad (2)$$

eqn (2) is a second order linear homogeneous eqn

Its characteristic eqn is

$$\boxed{p^2 + \frac{R}{L} p + \frac{1}{LC} = 0} \quad \text{--- (2) } \left[\because p = \frac{d}{dt} \right]$$

The root of this eqn

$$= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= \alpha \pm \beta$$

$$p_1 = \alpha + \beta \quad p_2 = \alpha - \beta$$

$$\alpha = -\frac{R}{2L} \quad \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


The soln of the differential eqn

$$\boxed{i = k_1 e^{p_1 t} + k_2 e^{p_2 t}} \quad \text{--- (3)}$$

where k_1, k_2 are constant whose values are calculated from boundary condn

Q. A constant voltage is applied to R-L series ckt at $t=0$ by closing a switch. The voltage drop across 'L' is 55V at $t=0$. It drops to 5V at $t=0.025$ sec, $L=2H$ find (a) the applied voltage (b) the value of R

Ans

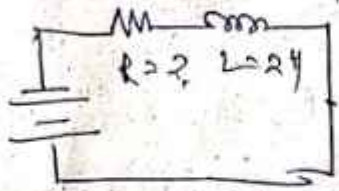

(a) At $t=0$, the entire voltage is dropped across inductor & no voltage is dropped across the resistor. So applied voltage

$$V = 25 \text{ V}$$

(b) At any instant voltage across inductor is 5V

$$V_L = V e^{-t/\tau}$$

$$\Rightarrow 5 = 25 e^{-\frac{0.025}{\tau}}$$

$$\Rightarrow \tau = 0.01553$$

$$\Rightarrow \frac{L}{R} = 0.01553$$

$$\Rightarrow R = \frac{L}{0.01553} = \frac{2}{0.01553} = 128.78 \Omega$$

$$\Rightarrow \boxed{R = 128.8 \Omega}$$

Q. The winding of an electromagnet has an inductance of 5H & resistance of 15 Ω . When it is connected to 20V DC supply calculate

(a) The steady state value of current flowing in the winding

(b) The time const. of the circuit

(c) The value of induced emf after 0.1 sec.

(d) The time for the current to rise to 85%.

of its final value.

(e) The value of current after 0.3 sec

Ans

(a) Given $R = 15 \Omega$, $L = 3H$, $V = 120V$.

Steady state current $I_0 = \frac{V}{R} = \frac{120}{15} = 8A$

(b) $\tau = \frac{L}{R} = \frac{3}{15} = 0.2 \text{ sec}$.

(c) The value of induced emf after 0.15 sec.

$$V_L = V e^{-t/\tau} = 120 \left(e^{-\frac{0.15}{0.2}} \right) = 72.8 \text{ V}$$

(d) Current at any instant during rise is

$$i = I_0 (1 - e^{-t/\tau})$$

$$\Rightarrow \frac{85}{100} I_0 = I_0 (1 - e^{-t/0.2})$$

$$\Rightarrow \boxed{t = 0.379 \text{ sec}}$$

$$(e) i = I_0 (1 - e^{-t/\tau}) = 8 (1 - e^{-\frac{0.3}{0.2}})$$

$$\Rightarrow \boxed{i = 6.21A}$$

Q An 8 μF capacitor is connected in series with 0.5 M Ω resistance across 200V supply calculate (a) initial charging current (b) the current and power developed across capacitor, 4 second after it connected to supply.

Ans

$$C = 8 \mu F = 8 \times 10^{-6} F$$

$$R = 0.5 M\Omega = 0.5 \times 10^6 \Omega$$

$$V = 200 \text{ volt}$$

(a) initial charging current $= \frac{V}{R}$
 $= \frac{200}{0.5 \times 10^6} = 4 \times 10^{-4} \text{ A}$

(b) time constant $= \tau = RC = 0.5 \times 10^6 \times 8 \times 10^{-6} = 4 \text{ sec}$

* The current across capacitor is 4 sec, after it is connected to the supply is

$$i = \frac{V}{R} e^{-t/\tau}$$

$$i = 4 \times 10^{-4} e^{-\frac{t}{4}}$$

$$i = 1.47 \times 10^{-4} \text{ A}$$

* The power developed across capacitor in 4 sec after it is connected to the supply is

$$V_C = V(1 - e^{-t/\tau})$$

$$\Rightarrow V_C = 200(1 - e^{-4/4}) = 126.44 \text{ volt}$$

Q2) The time constant of a coil was found to be 2.5 ms with a resistance of 100 Ω added in series, a new time constant of 0.5 ms was obtained. Find R & L of the coil.

Soln) Given time constant $\tau = \frac{L}{R} = 2.5 \text{ ms}$
 $R = 2.5 \times 10^3$
 when resistance (R) added the time constant.

$$\tau_1 = \frac{L}{R+100} = 0.5$$

$$\frac{\tau}{\tau_1} = \frac{2.5}{0.5}$$

$$\Rightarrow \frac{\frac{L}{R}}{\frac{L}{R+100}} = 5 \Rightarrow \frac{R+100}{R} = 5$$

$$\Rightarrow \boxed{R = 25 \Omega}$$

But given $\frac{L}{R} = 2.5 \times 10^{-3}$

So $L = 2.5 \times 10^{-3} \times R = 2.5 \times 10^{-3} \times 25$
 $= 62.5 \times 10^{-3} \text{ H}$

$L = 62.5 \times 10^{-3} \text{ H}$

Sl. No	Name of the element	Symbol	At $t=0$	At $t=t(b)$
1	Resistor			
2	Inductor			
3	Capacitor			
4	Inductance with initial current I_0			
5	Capacitance with initial voltage V_0			

Ae. Analysis

→ Admittance is defined as where Y is the admittance in siemens Z is the impedance measured in ohm.

→ Resistance is a measure of the opposition of a circuit to the flow of a steady current while impedance takes into account not only the resistance but also dynamic effect, known as reactance.

$Y = \frac{1}{Z}$

In R.L series ckt $\rightarrow Z = \sqrt{R^2 + X_L^2}$
 $X_L = \omega L = 2\pi fL$

In R.C. series ckt $\rightarrow Z = \sqrt{R^2 + X_C^2}$
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$

In R.L.C $Z = \sqrt{R^2 + (X_L - X_C)^2}$

\rightarrow Average value = $\frac{\text{Area under the curve.}}{\text{length of the base of the curve}}$

\rightarrow R.M.S value = $\sqrt{\frac{\text{Area of half cycle wave squared}}{\text{Half cycle base}}}$

\rightarrow Form factor \rightarrow The ratio of rms value to ~~the~~ average value of an alternating ~~quantity~~ quantity is known as form factor. It is represented by k_f

$$k_f = \frac{\text{R.M.S value}}{\text{Avg. value.}}$$

\rightarrow Peak factor \rightarrow The ratio of maximum value to the rms value of an alternating quantity is known as peak factor or amplitude factor. It is represented by k_a .

$$k_a = \frac{\text{maximum value}}{\text{R.M.S value.}}$$

Types of power

- 1) Active power / Real power / True power
 - 2) Reactive power / Pulsating power
 - 3) Apparent power $= |V| |I|$
 - 4) Complex power $= V I^*$
- $C I^* \rightarrow$ complex conjugate of I

* Instantaneous & Average power

\rightarrow In an a.c. ckt the power at any instant is called so.

\rightarrow It is equal to the product of the value of voltage and current at any instant.

\rightarrow In an a.c. ckt let the instantaneous value of the voltage & current

$$V = V_m \sin \omega t$$

$$I = I_m \sin (\omega t - \phi)$$

where ϕ = phase angle between V & I

\rightarrow Instantaneous power $p = v i$

$$= V_m \sin \omega t \times I_m \sin (\omega t - \phi)$$

$$= V_m \cdot I_m \sin \omega t \cdot \sin (\omega t - \phi)$$

$$= \frac{1}{2} V_m \cdot I_m [\cos \phi - \cos (2\omega t - \phi)]$$

$$\because \cos A \cdot \cos B = \frac{1}{2} [\sin(A+B) + \sin(A-B)]$$

$$= \frac{1}{2} V_m I_m \cos \phi - \frac{1}{2} V_m I_m \cos (2\omega t - \phi)$$

\Rightarrow The 2nd term of right hand side of the above eqn contains a double frequency 2ω , so the magnitude of the avg. value of the 2nd term is zero. It is because average of sinusoidal quantity of double frequency over a complete cycle is zero. Hence the 2nd term is avoided,

$$P_{av} = \frac{1}{2} V_m I_m \cos \phi$$

\rightarrow The instantaneous power is the avg. power in A.C circuit $P_{av} = \frac{1}{2} V_m I_m \cos \phi$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P_{av} = VI \cos \phi$$

$V = \frac{V_m}{\sqrt{2}}$ = rms value of the voltage in A.C ckt

$I = \frac{I_m}{\sqrt{2}}$ = rms value of current in A.C circuit

$$P = VI \cos \phi$$

ϕ is Active power

Reactive power

\rightarrow Reactive power generates from reactive element (inductor & capacitor)

\rightarrow The product of rms value of voltage & current

with the sine of the angle between them is called the reactive power in A.C circuit.

$$Q = VI \sin \phi$$

→ Reactive power for purely inductive ckt.

$$Q_L = V_L I_L = I^2 X_L = \frac{V_L^2}{X_L}$$

where $X_L = \text{Inductive reactance}$

$$X_L = \omega L = 2\pi fL$$

→ Reactive power for purely capacitive ckt

$$Q_C = V_C I_C = I^2 X_C = \frac{V_C^2}{X_C}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

Complex power

→ The product of r.m.s value of the voltage & current in a ckt is called complex power.

→ It is represented by 'S' & its unit VA


→ In complex form

$$S = P + jQ \quad (\text{for inductive ckt})$$

$$S = P - jQ \quad (\text{for capacitive ckt})$$

→ Magnitude of the complex power $S = \sqrt{P^2 + Q^2}$

Power triangle

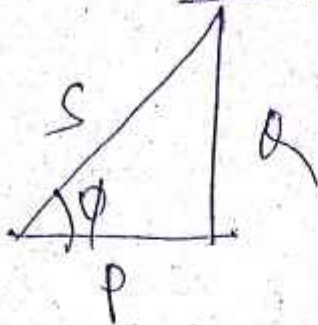

$$\tan \phi = (Q/P)$$

$$\phi = \tan^{-1} (Q/P)$$

Analysis of coupled circuit

Self inductance

When a current changes in a circuit, the magnetic flux linking the same circuit changes (in vice versa) and emf is induced in the circuit. This induced emf is proportional to the rate of change current.

$$V = L \frac{di}{dt} \quad \text{--- (1)}$$

V = induced voltage

$\frac{di}{dt}$ = Rate of change of current

L = const. of proportionality called self inductance.

we know $L = \frac{N \phi}{i}$ --- (2)

$N =$ no. of turns in the circuit

$\phi =$ flux linkage.

Substituting eq(2) in eq(1) we get

$$V = \frac{L d \left(\frac{NI}{L} \right)}{dt}$$

$$= L \times \frac{L}{L} \times N \frac{d\phi}{dt}$$

$$\boxed{V = N \frac{d\phi}{dt}} \quad \text{--- (3)}$$

comparing eq(1) & (3)

$$L \frac{di}{dt} = N \frac{d\phi}{dt}$$

$$\Rightarrow \boxed{L = N \frac{d\phi}{di}} \quad \text{--- (4)}$$

Mutual Inductance,


when 2 coils carry currents i_1 & i_2 each coil will have leakage flux ϕ_{11} & ϕ_{22}

coil 1 & coil-2 respectively as well as mutual flux ϕ_{21} .

the flux of coil-2 links coil-1 OR ϕ_{12} , the flux of coil-1 links coil-2.

The induced voltage of coil-2 is
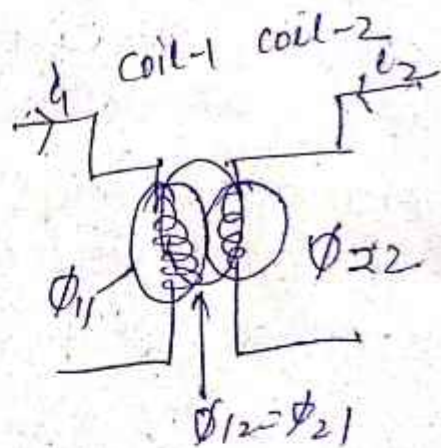
$$V_{L_2} = N_2 \frac{d\phi_{12}}{dt} \quad \text{--- (1)}$$



Again since ϕ_{12} is related to the current of coil-2 & the induced voltage is proportional to the rate of change of i_2 .

$$V_{12} = M_2 \frac{di_2}{dt} \quad \text{--- (2)}$$

where M is the mutual inductance between the 2 coils

comparing eqn (1) & (2)

$$M \frac{di_2}{dt} = N_2 \frac{d\phi_{12}}{dt}$$

$$\Rightarrow \boxed{M = N_2 \frac{d\phi_{12}}{di_2}} \quad \text{--- (3)}$$

$$\text{Similarly } \boxed{M = N_1 \frac{d\phi_{21}}{di_1}} \quad \text{--- (4)}$$

when the coils are linked with air medium the flux & current are linearly related

$$\left. \begin{aligned} M &= N_2 \frac{\phi_{12}}{i_1} \\ M &= N_1 \frac{\phi_{21}}{i_2} \end{aligned} \right\} \quad \text{--- (5)}$$

Co-efficient of coupling (K)

It is defined as the fraction of total flux that links the coils

$$\boxed{k = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2}}$$

The max^m value of k is unity

From eqⁿ (1)

$$M^2 = N_1 N_2 \frac{\phi_{12} \phi_2}{l_1 l_2}$$



$$= N_1 N_2 \frac{k \phi_1 k \phi_2}{l_1 l_2}$$

$$= k^2 \frac{N_1 \phi_1}{l_1} \cdot \frac{N_2 \phi_2}{l_2}$$

$$M^2 = k^2 L_1 L_2$$

$$\Rightarrow M = k \sqrt{L_1 L_2}$$


For series connection of coupled coils

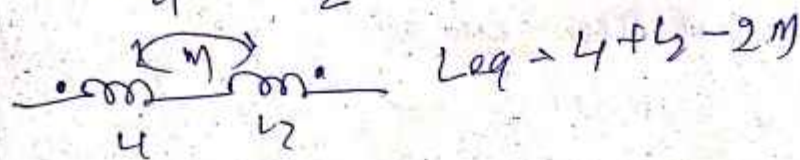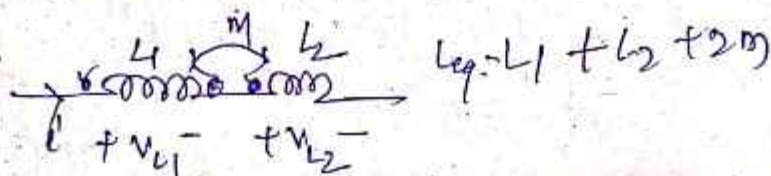

For parallel connection

(1) For adding $\rightarrow L_{eff} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$

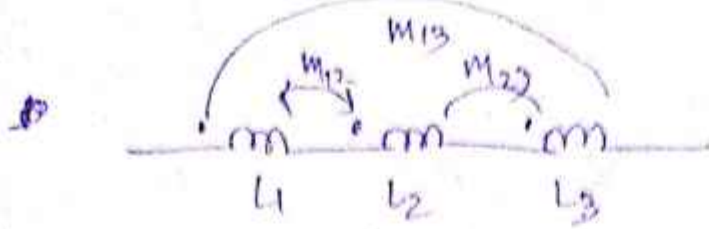(2) Parallel opposing $L_{eff} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$



for coil 1 $\rightarrow L_1 + M_{12} + M_{13}$

coil 2 $\rightarrow L_2 + M_{12} + M_{23}$

coil 3 $\rightarrow L_3 + M_{13} + M_{23}$


The net inductance =

$$L_1 + M_{12} + M_{13} + L_2 + M_{12} + M_{23}$$

$$+ L_3 + M_{23} + M_{13}$$

$$= L_1 + L_2 + L_3 + 2(M_{12} + M_{23} + M_{13})$$

Series Resonance,

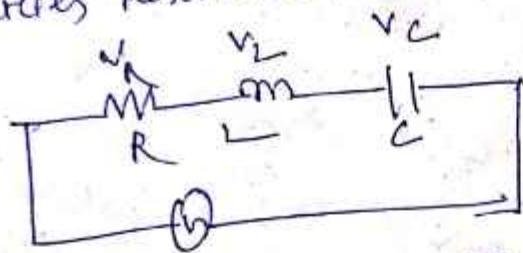

$$I = \frac{V}{Z}$$

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\omega L - \frac{1}{\omega C}$$

$$= R + j(X_L - X_C)$$

Let f_0 or ω_0 be the frequency at $X_L = X_C$.

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \text{Hz}$$

Q factor $Q = \frac{V_L}{V} = \frac{V_C}{V}$

Q1 Bandwidth of series Resonating circuit & its relation with Q.

Ans The frequency band width in the limits of lower and upper power frequency is called the bandwidth of the resonant circuit.

$$X = \pm (X_L - X_C) = R$$

$$R = \pm \left(\omega L - \frac{1}{\omega C} \right) = \pm X$$

Let f_1 be the frequency when the net circuit reactance be $-ve$ and f_2 be frequency when the net circuit reactance is $+ve$.

$$\text{Then } (\omega_2 L - \frac{1}{\omega_2 C}) = R \quad \text{--- (1)}$$

$$(\omega_1 L - \frac{1}{\omega_1 C}) = -R \quad \text{--- (2)}$$

Adding eqⁿ (1) & (2)

$$(\omega_2 + \omega_1)L - \frac{1}{C} \left(\frac{1}{\omega_2} + \frac{1}{\omega_1} \right) = 0$$

$$\Rightarrow (\omega_2 + \omega_1)L - \frac{1}{C} \left(\frac{\omega_2 + \omega_1}{\omega_1 \omega_2} \right) = 0$$

$$\Rightarrow L = \frac{1}{C} * \frac{1}{\omega_1 \omega_2}$$

Again subtracting eqⁿ (2) from eqⁿ (1).

$$(\omega_2 - \omega_1)L + \frac{1}{C} \left(\frac{1}{\omega_1} - \frac{1}{\omega_2} \right) = 2R$$

$$\Rightarrow (\omega_2 - \omega_1)L + \frac{1}{C} \left(\frac{\omega_2 - \omega_1}{\omega_2 \omega_1} \right) = 2R \quad \text{--- (3)}$$

Dividing eqⁿ (3) by L

$$(\omega_2 - \omega_1) + \frac{1}{LC} \left(\frac{\omega_2 - \omega_1}{\omega_2 \omega_1} \right) = \frac{2R}{L}$$

$$\Rightarrow (\omega_2 - \omega_1) + \frac{1}{LC} \left(\frac{\omega_2 - \omega_1}{1/\mu} \right) = \frac{2R}{L}$$

$$\Rightarrow 2(\omega_2 - \omega_1) = \frac{2R}{L}$$

$$\Rightarrow (\omega_2 - \omega_1) = \frac{R}{L} \quad \text{--- (4)}$$

$$\Rightarrow \boxed{f_2 - f_1 = \frac{1}{2\pi} \frac{R}{L}}$$

we know $Q = \omega_0 \frac{L}{R} \Rightarrow \frac{R}{L} = \frac{\omega_0}{Q} \quad \text{--- (5)}$



Comparing with eqn (4)

$$\frac{\omega_0}{Q} = \omega_2 - \omega_1$$

$$\Rightarrow Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1}$$

$$\Rightarrow \boxed{Q = \frac{f_0}{\text{Bandwidth}} = \frac{\text{Resonant frequency}}{\text{Bandwidth}}}$$

Parallel Resonance

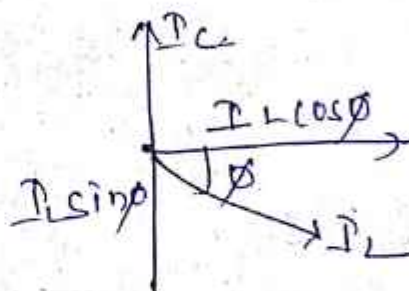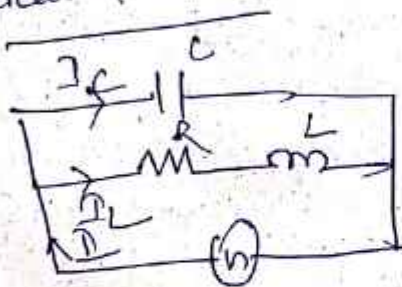

$$Y = Y_1 + Y_2$$

$$= \frac{j}{X_C} + \frac{1}{R + jX_L}$$

$$= \frac{j}{X_C} + \frac{R - jX_L}{R^2 + X_L^2}$$

$$= \frac{R}{R^2 + X_L^2} + j \left(\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right)$$

At resonance the imaginary part must be zero

$$\frac{1}{X_C} = \frac{X_L}{R^2 + X_L^2}$$

$$\Rightarrow \omega_0 C = \frac{\omega_0 L}{R^2 + \omega_0^2 L^2}$$

$$\Rightarrow R^2 + \omega_0^2 L^2 = \frac{1}{C}$$

$$\Rightarrow \omega_0^2 L^2 = \frac{1}{C} - R^2$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{L} \sqrt{\frac{L}{C} - R^2}}$$

$$f = \frac{1}{2\pi L} \sqrt{\frac{1}{C} - R^2}$$

$$Z = R + j\omega L$$

$$Z_L = \sqrt{R^2 + (\omega L)^2} = \sqrt{R^2 + \frac{L}{C} - R^2}$$

$$Z_L = \sqrt{\frac{L}{C}}$$

Resonant current $I = \frac{V}{\sqrt{LC}}$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Laplace Transforms

Let $f(t)$ be a function of time which is zero for $t < 0$ and which is arbitrary defined for $t > 0$ subject to some condition. Then the Laplace transform of the function $f(t)$, denoted by $F(s)$ is defined as

$$L[f(t)] = F(s) = \int_0^{\infty} f(t) \cdot e^{-st} \cdot dt.$$

1 \rightarrow $u(t) \rightarrow$ unit step $\rightarrow \frac{1}{s}$

2 \rightarrow $u(t-T) \rightarrow$ unit step by function delay by $T \rightarrow \frac{e^{-sT}}{s}$

3 \rightarrow $\delta(t) \rightarrow$ unit impulse $\rightarrow 1$

4 \rightarrow $e^{at} \rightarrow$ exponential $\rightarrow \frac{1}{s-a}$

5 \rightarrow $e^{-at} \rightarrow$ exponential $\rightarrow \frac{1}{s+a}$

6 \rightarrow $\sin \omega t \rightarrow$ sine function $\rightarrow \frac{\omega}{s^2 + \omega^2}$

7 \rightarrow $\cos \omega t \rightarrow$ cosine function $\rightarrow \frac{s}{s^2 + \omega^2}$

8 \rightarrow t^n ($n = 1, 2, 3, \dots$) \rightarrow ramp function $\rightarrow \frac{n!}{s^{n+1}}$

9 \rightarrow $t \rightarrow$ unit ramp function $\rightarrow \frac{1}{s^2}$

Convolution integral.

→ Convolution of 2 real function corresponds to multiplication of their respective functions.

$$\rightarrow \text{if } \mathcal{L}[f_1(t)] = F_1(s) \text{ \& } \mathcal{L}[f_2(t)] = F_2(s)$$

Convolution is defined by

$$\mathcal{L}[f_1(t) * f_2(t)] = F_1(s) \cdot F_2(s) \quad (1)$$

→ The 2 functions $f_1(t)$ & $f_2(t)$ are multiplied in such a manner that one is continuously moving with time 't' relative to other.

$$\text{i.e. } f_1(t) * f_2(t) = \int_0^t f_1(t-\tau) \cdot f_2(\tau) d\tau \quad (2)$$

The statement of the mathematical expression given in expression (1) is called convolution theorem.

$$\text{let } \mathcal{L}[f_1(t) * f_2(t)] = F(s)$$

$$F(s) = \int_0^{\infty} [f_1(t) * f_2(t)] e^{-st} dt$$

$$\rightarrow F(s) = \int_{t=0}^{\infty} \left[\int_{\tau=0}^t f_1(t-\tau) \cdot f_2(\tau) \cdot d\tau \right] \cdot e^{-st} dt \quad (3)$$

Inverse Laplace theorem, (I.L.T)

→ The inverse Laplace theorem is the transformation of a Laplace transform into a function of time.

$$\rightarrow L^{-1}[f(s)] = f(t)$$

Q1 Determine I.L.T for $F(s) = \frac{s+1}{s(s+2)}$

$$\text{given } f(s) = \frac{s+1}{s(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+2}$$

$$A = (s \times f(s)) \Big|_{s=0} = s \times \frac{s+1}{s(s+2)} \Big|_{s=0} = \frac{1}{2}$$

$$B = (s+2) \times f(s) \Big|_{s=-2} = (s+2) \times \frac{s+1}{s(s+2)} \Big|_{s=-2} = \frac{1}{2}$$

$$f(s) = \frac{1}{2} \cdot \frac{1}{s} + \frac{1}{2} \cdot \frac{1}{s+2}$$

Taking inverse Laplace of above function,
for next step $f(t) = \frac{1}{2} + \frac{1}{2} \cdot e^{-2t} \quad t > 0$

Q1 $f(s) = \frac{2s+1}{(s+1)(s+2)(s+3)}$

Solⁿ $f(s) = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{s+3}$

$$A = (s+1) \times f(s) \Big|_{s=-1} = (s+1) \times \frac{2s+1}{(s+1)(s+2)(s+3)} = \frac{-1}{2}$$

$$B = (s+2) \times F(s) \Big|_{s=-2} = (s+2) \times \frac{2s+1}{(s+1)(s+2)(s+3)} \Big|_{s=-2} = 3$$

$$C = (s+3) \times F(s) \Big|_{s=-3} = (s+3) \times \frac{2s+1}{(s+1)(s+2)(s+3)} = -5/2$$

$$F(s) = \frac{(-1/2)}{s+1} + \frac{3}{s+2} + \frac{(-5/2)}{s+3}$$

we take I.L.T of above eq) we get

$$f(t) = -\frac{1}{2} e^{-t} + 3e^{-2t} - \frac{5}{2} e^{-3t}$$

Transfer function Representation

→ It is the ratio of Laplace transform of output signal or response to the Laplace transform of input signal or response taking all initial conditions are zero.

$$T.F = G(s) = \frac{V_2(s)}{V_1(s)}$$

$$Z(s) = \frac{V(s)}{I(s)} \rightarrow \text{Impedance function}$$


$$Y(s) = \frac{I(s)}{V(s)} \rightarrow \text{Admittance function}$$

In time domain

$$v(t) = R i(t)$$

In frequency domain


$$V(s) = R I(s)$$

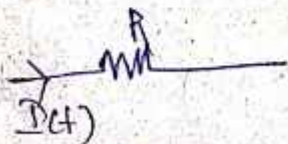

$$\text{---} \xrightarrow{I(t)} \text{---} \quad v(t) = L \frac{dI(t)}{dt} \rightarrow v(s) = Ls I(s)$$

$$\text{---} \xrightarrow{I(t)} \text{---} \quad v(t) = \frac{1}{C} \int I(t) dt \rightarrow v(s) = \frac{1}{Cs} I(s)$$

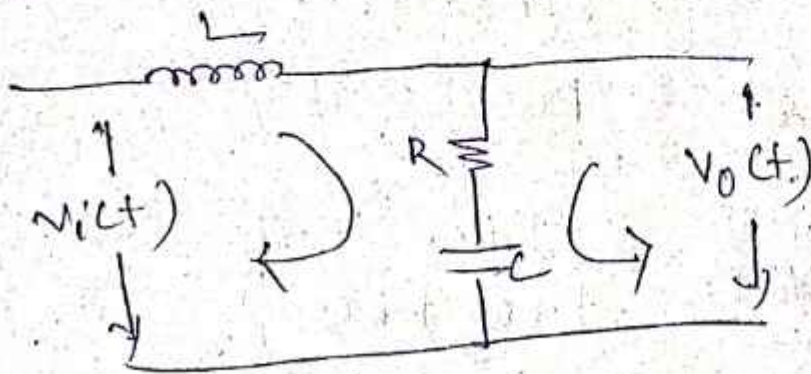Q.1) calculate the transfer function of given figure



Ans Applying KVL in input loop

$$v_i(t) = L \frac{dI(t)}{dt} + RI(t) + \frac{1}{C} \int I(t) dt \quad \text{--- (1)}$$

Applying KVL in op. loop

$$v_o(t) = RI(t) + \frac{1}{C} \int I(t) dt \quad \text{--- (2)}$$

Taking L.T. of above eq we get

$$\begin{aligned} \text{from eq (1)} \rightarrow v_i(s) &= Ls I(s) + RI(s) + \frac{1}{Cs} I(s) \\ &= I(s) \left[R + Ls + \frac{1}{Cs} \right] \quad \text{--- (3)} \end{aligned}$$

from eq (2)

$$\begin{aligned} v_o(s) &= RI(s) + \frac{1}{Cs} I(s) \\ &= I(s) \left[R + \frac{1}{Cs} \right] \quad \text{--- (4)} \end{aligned}$$

Transfer function $G(s) = \frac{V_o(s)}{V_i(s)}$

$$\frac{V_o(s)}{V_i(s)} = \frac{I(s) \left[R + \frac{1}{Cs} \right]}{I(s) \left[R + Ls + \frac{1}{Cs} \right]}$$

$$= \frac{RCS + 1}{RCS + Ls^2 + 1}$$

$$\boxed{G(s) = \frac{V_o(s)}{V_i(s)} = \frac{1 + RCS}{1 + RCS + Ls^2}}$$

Initial value theorem

→ Here we can find out the initial value of time function $f(t)$.

$$\boxed{f(0) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s \cdot F(s)}$$

→ The only restriction is that $f(t)$ must be continuous or the most, a step ~~transition~~ discontinuity at $t=0$.

Final value theorem

$$F(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s \cdot F(s)$$

→ The only restriction is that the root of the denominator polynomial of $F(s)$, i.e. pole of $F(s)$ have $-ve$ or 0 value.

Poles and zeros

$$\frac{C(s)}{R(s)} = G(s) = \frac{k(s+z_1)(s+z_2)(as^2+bs+c)}{(s+p_1)(s+p_2)(As^2+Bs+C)}$$

$k = \frac{bm}{an}$ is known as the gain factor 's' is the complex frequency.

Poles → The poles of $G(s)$ are those values of 's' which make $G(s)$ tend to infinity. For eq. in eqn (1) we have poles at $s = -p_1$, $s = -p_2$ and pairs of poles at $s = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$.

Zeros The zeros of $G(s)$ are those values of 's' which make $G(s)$ tends to zero. For eq. in eqn (1) we have zeros $s_1 = -z_1$, $s_2 = -z_2$ and pairs of zero's at $s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$.

* If either poles and zero coincide then such type of pole and zero are called multiple pole or multiple zero, otherwise they are known as simple pole or simple zero.

Q1) Determine pole and zero of given function

$$F(s) = \frac{s(s+1)}{(s+2)(s+4)}$$

Ans zero - $s=0, s=-1$


pole $s=-2, s=-4$

Q2) Draw the pole and zero of $F(s) = \frac{s}{(s+2)(s+3)}$

Soln) zeros $s=0$

pole $s=-2, -3$

Plot

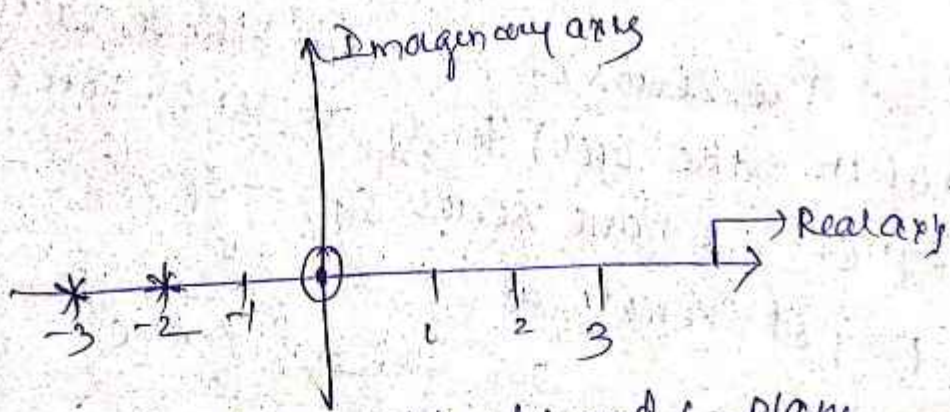


left half s-plane right hand s-plane
(s-plane)

Pole denoted as (*)

zero denoted as (o)

Two port Network

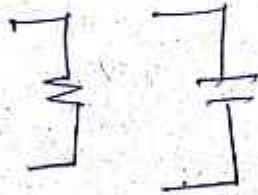- 1) Port \rightarrow A pair of terminal is known as port.
2) Single port Network \rightarrow If a n/w consists of one pair of terminal or 2 pairs of terminal is known as single phase port N/w.




\rightarrow 2 port Network, — The n/w having 2 pairs of terminal or four terminal is known as 2 port network.



\rightarrow In case of 2 port Network if one pair act as input (1-1') and the other pair act as output port (2-2')

N-port Network \rightarrow If a network having n-pair of terminals or 2n terminal is known as n-port n/w.

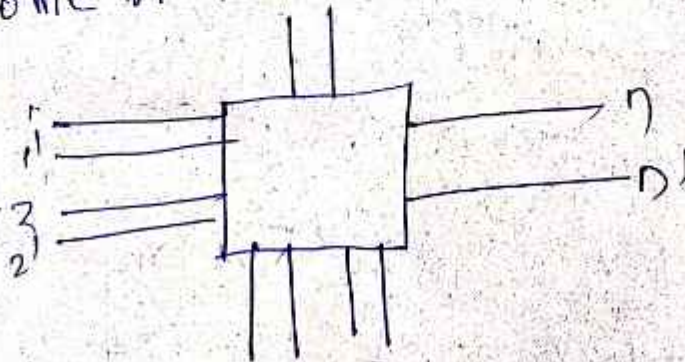\rightarrow In n port network some of them act as i/p port and some of them act as o/p port.



Parameter Representing of 2 port network

The relationship between V_1, I_1, V_2, I_2 can be represented in different parameters from the Z-parameter, Y-parameter, h-parameter, ABCD (transmission) parameters.

Z-parameter (Open circuit parameter)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$



The parameters can be obtained as:

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

→ The Z-parameter are also known as open circuit parameter because all the parameters are obtained by opening input port ($I_2=0$) or opening the output port ($I_1=0$)

Y-parameter (short-circuit parameter)

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

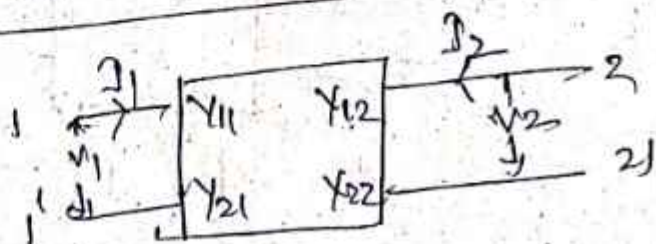

The parameters can be obtained as

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$


$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

The above parameters are also known as short circuit parameters because we can obtain all the parameters by short circuiting the i/p port ($V_1=0$) or by short circuiting the o/p port ($V_2=0$).

Representation of h-parameter (Hybrid parameter)

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

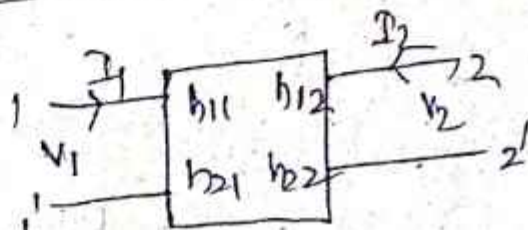

The parameters can be obtained as

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$


$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

The h-parameters are obtained by the combination of z-parameters and y-parameters and constant for which, they are called as hybrid parameters.

Representation of ABCD parameters (Transmission line parameters)

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

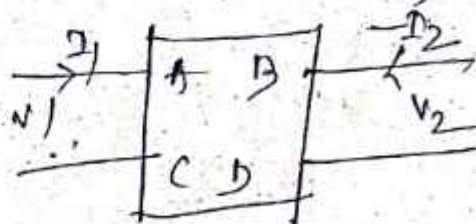

The parameters can be obtained as

$$A \rightarrow \frac{V_1}{V_2} \Big|_{I_2=0}$$


$$B \rightarrow \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$C \rightarrow \frac{I_1}{V_2} \Big|_{I_2=0}$$

$$D \rightarrow \frac{I_1}{-I_2} \Big|_{V_2=0}$$

The above 4 parameters calculated are used in transmission line for which they are known as transmission parameters.

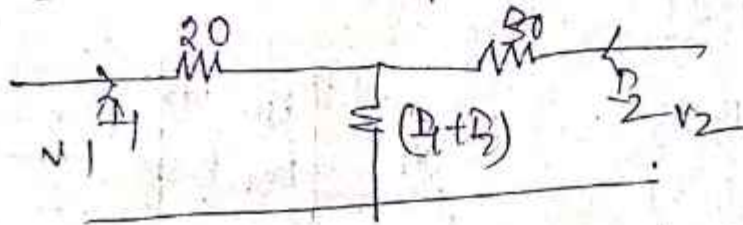Q Determine Z-parameters for the network.



Sol As per formula

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = \frac{20 \cdot I_1 + 10 \cdot I_1}{I_1} = \frac{30 I_1}{I_1}$$

$$Z_{11} = 30 \Omega$$

$$Z_{21} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$= \frac{10 I_2}{I_2} = 10 \Omega$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{10 I_2 + 30 I_2}{I_2}$$

$$Z_{22} = 40 \Omega \Big|_{I_2=0} = 40 \Omega$$

$$Z_{22} = 40 \Omega$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$= \frac{10 I_2}{I_2}$$

$$Z_{12} = 10 \Omega$$

Condition for symmetry

→ A 2 port network is said to be symmetric if the port can be interchanged without changing port voltage or current.

(a) In term of Z parameter $\Rightarrow Z_{11} = Z_{22}$

(b) In " Y " $\Rightarrow Y_{11} = Y_{22}$

(c) In " h " $\Rightarrow \Delta h = 1$

OR
$$\begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1$$

(d) " " ABCD " $\Rightarrow \boxed{A = D}$

Condition for Reciprocity

→ A network is said to be reciprocal if the ratio of the response to be excitation remains same, to interchange of the position of the excitation and response in the network.

(a) In term of Z parameter $\Rightarrow Z_{12} = Z_{21}$

(b) " " Y " $\Rightarrow Y_{12} = Y_{21}$


(c) " " h " $\Rightarrow h_{12} = -h_{21}$

(d) " " ABCD " $\Rightarrow \Delta T = 1$

OR $AD - BC = 1$

OR $\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$

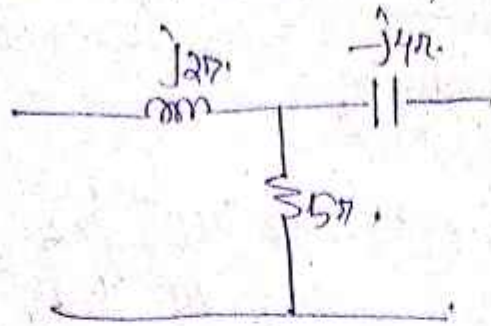
Q. For the network shown in fig calculate T-parameters.



Soln T-parameter eqn

$$V_1 = AV_2 - B I_2 \quad \text{--- (1)}$$
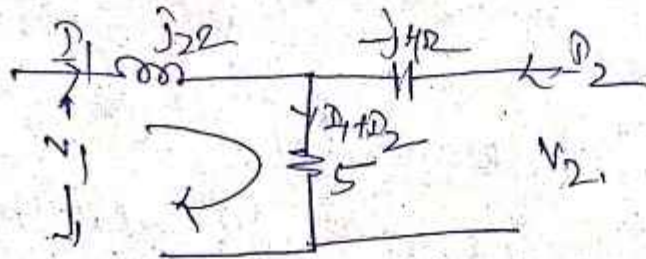
$$I_1 = CV_2 - D I_2 \quad \text{--- (2)}$$



By KVL in loop (1) $-j2 \times I_1 - 5(I_1 + I_2) + V_1 = 0$

$$\Rightarrow V_1 = 5(I_1 + I_2) - j2 I_1 \quad \text{--- (3)}$$

By KVL in loop (2)

$$j4 I_2 - 5(I_1 + I_2) + V_2 = 0$$

$$\Rightarrow V_2 = 5 I_1 + (5 - j4) I_2 \quad \text{--- (4)}$$

Putting I_1 from eqn (4) in eqn (3) we get

$$V_1 = 5(I_1 + I_2) - j2 I_1$$

$$\Rightarrow V_1 = \left(\frac{5 + j2}{5}\right) V_2 - \left[\frac{(5 + j2)(5 - j4)}{5} - 5\right] I_2 \quad \text{--- (5)}$$

For making as eqn (2) rearrange eqn (1) we get

$$I_1 = \frac{1}{5} V_2 - \left(\frac{5-j4}{5}\right) I_2 \quad \text{--- (6)}$$

To obtain T-parameters comparing eqn (1) & eqn (2)

$$\begin{aligned} \text{Cor } A &= \left(\frac{5+j2}{5}\right) & B &= \frac{(5+j2)(5-j4) - 5}{5} \\ & & &= \frac{8-j10}{5} \end{aligned}$$

Comparing eqn (2) & (6) we get


$$C = \left(\frac{1}{5}\right) \quad D = \left(\frac{5-j4}{5}\right)$$

Interconnection of 2-port networks

- (1) series connection
- (2) cascade connection
- (3) parallel connection

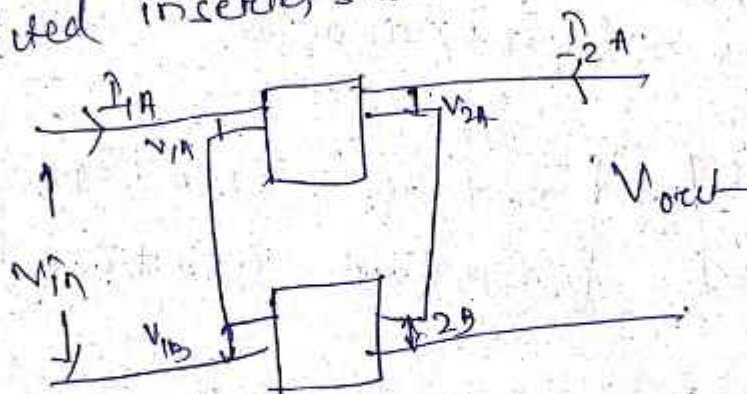(1) series connection

Let networks A & B be the 2 port network connected in series shown in fig.



For network A

$$V_{1A} = Z_{11A} I_{1A} + Z_{12A} I_{2A}$$

$$V_{2A} = Z_{21A} I_{1A} + Z_{22A} I_{2A}$$

For network B

$$V_{1B} = Z_{11B} I_{1B} + Z_{12B} I_{2B}$$

$$V_{2B} = Z_{21B} I_{1B} + Z_{22B} I_{2B}$$

The interconnection results

$$\begin{array}{l|l} I_1 = I_{1A} = I_{1B} & V_1 = V_{1A} + V_{1B} \\ I_2 = I_{2A} = I_{2B} & V_2 = V_{2A} + V_{2B} \end{array}$$

$$V_1 = V_{1A} + V_{1B}$$

$$\Rightarrow V_1 = (Z_{11A} I_{1A} + Z_{12A} I_{2A}) + (Z_{11B} I_{1B} + Z_{12B} I_{2B})$$

$$\Rightarrow V_1 = I_1 (Z_{11A} + Z_{11B}) + I_2 (Z_{12A} + Z_{12B}) \quad (1)$$

And $V_2 = V_{2A} + V_{2B}$

$$V_2 = (Z_{21A} I_{1A} + Z_{22A} I_{2A}) + (Z_{21B} I_{1B} + Z_{22B} I_{2B})$$

$$V_2 = I_1 (Z_{21A} + Z_{21B}) + I_2 (Z_{22A} + Z_{22B}) \quad (2)$$

Thus we get eqn (1) & (2)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11A} + Z_{11B} & Z_{12A} + Z_{12B} \\ Z_{21A} + Z_{21B} & Z_{22A} + Z_{22B} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$\text{Hence } [Z] = [Z_A] + [Z_B]$$

Thus it has been observed that the overall Z parameter matrix for series connected two port network is simply the sum of Z matrices of each individual network.

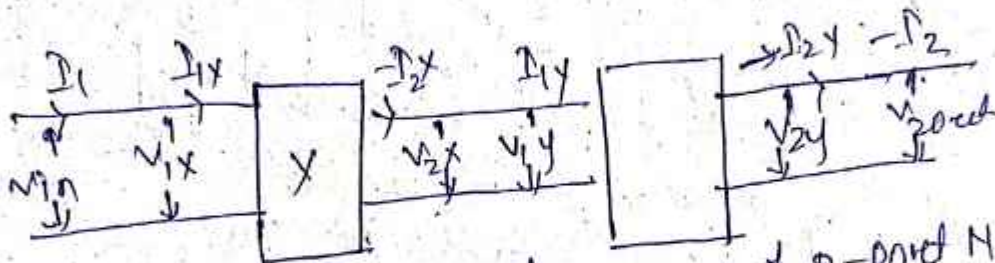(2) cascade connection

→ ABCD parameters are highly useful in characteristic cascade of 2-port network.

→ Let X & Y be 2 networks connected in cascade



(Cascade connected 2 no. of 2-port Network)

For network X

$$V_{1x} = A_x V_{2x} - B_x I_{2x}$$

$$I_{1x} = C_x V_{2x} - D_x I_{2x}$$

For network Y

$$V_{1y} = A_y V_{2y} - B_y I_{2y}$$

$$I_{1y} = C_y V_{2y} - D_y I_{2y}$$

For the cascade connection

$$I_1 = I_{1x} ; -I_{2x} = I_{1y} ; I_2 = I_{2y}$$

$$V_1 = V_{1x} ; V_{2x} = V_{1y} ; V_2 = V_{2y}$$

The overall transmission parameter for the combined network as show in fig (above) in matrix form

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1x} \\ I_{1x} \end{bmatrix} = \begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} V_{2x} \\ -I_{2x} \end{bmatrix}$$

$$= \begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$= \begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$= \begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} A_y & B_y \\ -C_y & D_y \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


where $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_x & B_x \\ C_x & D_x \end{bmatrix} \begin{bmatrix} A_y & B_y \\ C_y & D_y \end{bmatrix}$

The overall ABCD parameter network matrix for cascaded n/w is then the matrix product of ABCD matrices of individual network.

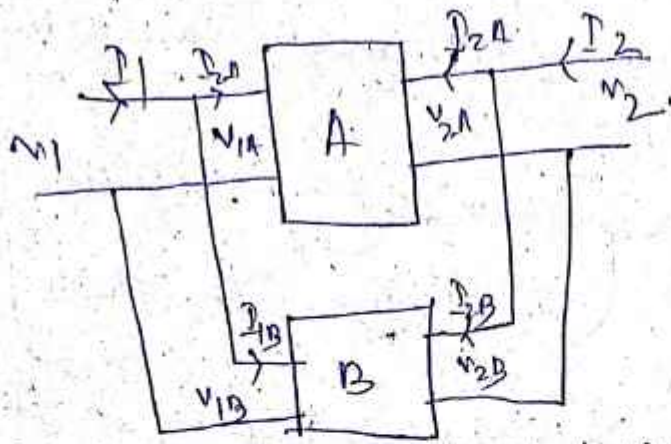(3) Parallel connection

→ Let A & B network be connected in parallel as shown in fig,

→ γ -parameter representation is very much useful.



(Parallel connection of two 2-port network)

For network A

$$I_{1A} = Y_{11A} V_{1A} + Y_{12A} V_{2A}$$

$$I_{2A} = Y_{21A} V_{1A} + Y_{22A} V_{2A}$$

Network B

$$I_{1B} = Y_{11B} V_{1B} + Y_{12B} V_{2B}$$

$$I_{2B} = Y_{21B} V_{1B} + Y_{22B} V_{2B}$$

For the parallel connection

$$V_1 = V_{1A} = V_{1B}$$

$$V_2 = V_{2A} = V_{2B}$$

$$I_1 = I_{1A} + I_{1B}$$

$$I_2 = I_{2A} + I_{2B}$$

$$\text{Thus } I_1 = I_{1A} + I_{1B}$$

$$\Rightarrow I_1 = (Y_{11A} V_{1A} + Y_{12A} V_{2A}) + (Y_{11B} V_{1B} + Y_{12B} V_{2B})$$

$$\Rightarrow I_1 = (Y_{11A} + Y_{11B}) V_1 + (Y_{12A} + Y_{12B}) V_2 \quad \text{--- (1)}$$

$$\text{And } I_2 = I_{2A} + I_{2B}$$


$$\Rightarrow I_2 = (Y_{21A} V_{1A} + Y_{22A} V_{2A}) + (Y_{21B} V_{1B} + Y_{22B} V_{2B})$$

$$\Rightarrow I_2 = (Y_{21A} + Y_{21B}) V_1 + (Y_{22A} + Y_{22B}) V_2 \quad \text{--- (2)}$$

Finally from eqn. (1) and (2) in matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11A} + Y_{11B} & Y_{12A} + Y_{12B} \\ Y_{21A} + Y_{21B} & Y_{22A} + Y_{22B} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

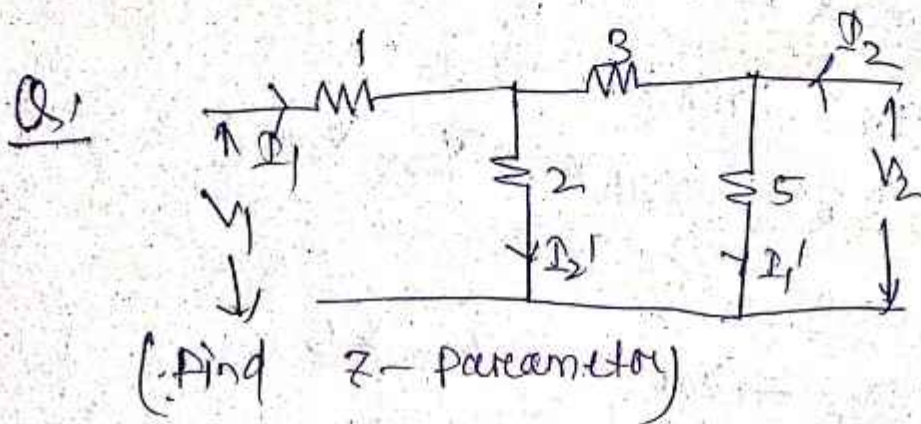→ The overall Y parameter matrix is then simply the summation of Y matrices of each individual 2 port network.



Soln Case-1 ($I_2 = 0$)

$$Z_{11} = (8 \parallel 2) + 1 = 2.6 \Omega \quad I_1 = \frac{2}{10} \times I_1 = I_1/5$$

$$\Rightarrow V_2 = 5 I_1' = 5 \times \frac{I_1}{5} = I_1$$

$$\Rightarrow Z_{21} = \frac{V_2}{I_1} = 1 \Omega$$

Case-2 ($I_1 = 0$)

$$Z_{22} = 5 \parallel 5 = \frac{5 \times 5}{5+5} = 2.5 \Omega$$

$$I_2' = \frac{5}{10} I_2 = \frac{I_2}{2}$$

$$V_1 = 2 \times I_2' = 2 \times \frac{I_2}{2} = I_2$$

$$Z_{12} = \frac{V_1}{I_2} = 1 \Omega$$

(AM)

Ex 10.9

A series R-L-C ckt with values: $R = 10\Omega$, $L = 0.2\text{H}$ & $C = 100\mu\text{F}$ is excited from a D.C source of 50V. by sudden switching ON of a key at time $t = 0\text{s}$. Find the expression for the resulting current.

Ans $R = 10\Omega$ $L = 0.2\text{H}$ $C = 100\mu\text{F}$ $V = 50\text{V}$

$$V = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Taking Laplace transform.

$$\frac{V}{s} = R I(s) + sL I(s) - I(0) + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{q(0)}{s} \right]$$

There is no initial current in the inductor & initial charge on capacitor

$$\frac{V}{s} = R I(s) + sL I(s) + \frac{1}{C} \left[\frac{I(s)}{s} \right]$$

$$[\because I(0) = 0, q(0) = 0]$$

$$\frac{V}{s} = \left[R + sL + \frac{1}{Cs} \right] I(s)$$

$$V C = [R C s + s^2 L C + 1] I(s)$$

$$V C = L C \left[s^2 + \frac{R}{L} s + \frac{1}{L C} \right] I(s)$$

$$\Rightarrow \frac{\frac{V}{L}}{s^2 + (R/L)s + 1} = I(s)$$

$$\Rightarrow I(s) = \frac{50/0.2}{s^2 + \frac{10}{0.2}s + \frac{1}{0.2 \times 100 \times 10^{-6}}}$$

$$= \frac{250}{s^2 + 50s + 5 \times 10^4}$$

Taking inverse Laplace transform

$$I(s) = \frac{250}{s^2 + 2.5 \cdot 25 + (25)^2 + 5 \times 10^4 - (25)^2}$$

$$= \frac{250}{(s+25)^2 + (222.2)^2}$$

$$= \frac{250}{(s+25)^2 + (222.2)^2} \times \frac{222.2}{222.2}$$

$$I(t) = 1.25 e^{-25t} \sin 222.2t$$

Q. A series capacitor when connected in series with a coil having 40Ω resistance, resonates at 1000 Hz . Find the inductance of the coil. Also obtain the circuit current if the applied voltage is 100 V . Also calculate the voltage across the capacitor and the capacitor and the coil at resonance.

Sol

At resonance:

$$X_L = X_C$$

$$\Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$

$$L = \frac{1}{4\pi^2 f^2 C}$$

$$= \frac{1}{4\pi^2 \times 1000^2 \times 50 \times 10^{-6}} = 0.5 \text{ mH}$$

$$I_0 = \frac{V}{Z} = \frac{V}{R} \text{ at resonance,}$$

$$= \frac{100}{40} = 2.5 \text{ A.}$$

$$\text{Power loss of the coil} = I_0^2 R = 2.5^2 \times 40 = 250 \text{ W.}$$

$$\text{Again } V_L = I_0 X_L = 2.5 \times \frac{1}{2\pi f_0 L}$$

$$= 2.5 \times \frac{1}{2\pi \times 1000 \times 50 \times 10^{-6}}$$

$$= 7.96 \text{ V}$$

$$X_L = \omega L = 2\pi \times 1000 \times 0.5 \times 10^{-3}$$

$$= 3.142$$

$$V_{\text{coil}} = I_0 Z_{\text{coil}} \text{ (At resonance)}$$

$$= 2.5 \sqrt{40^2 + 3.142^2}$$

$$= 100.31 \text{ V}$$